 


Single Cycle RV-32I Processor



By Mostafa Mohamed Farhan

Introduction

In this project, you are required to implement a 32-bit single-cycle microarchitecture RISC-V processor based on Harvard Architecture. The single cycle microarchitecture executes an entire instruction in one cycle. In other words, instruction fetch, instruction decode, execute, write back, and program counter update occurs within a single clock cycle.

Objective

Referring to figure one, you are required to write the RTL Verilog files for all sub modules of the RISC-V processor (e.g. Register File, Instruction Memory, etc.). Then, implementing the top module of the RISC-V processor. Finally, you will configure this processor on Cyclone® IV FPGA device.

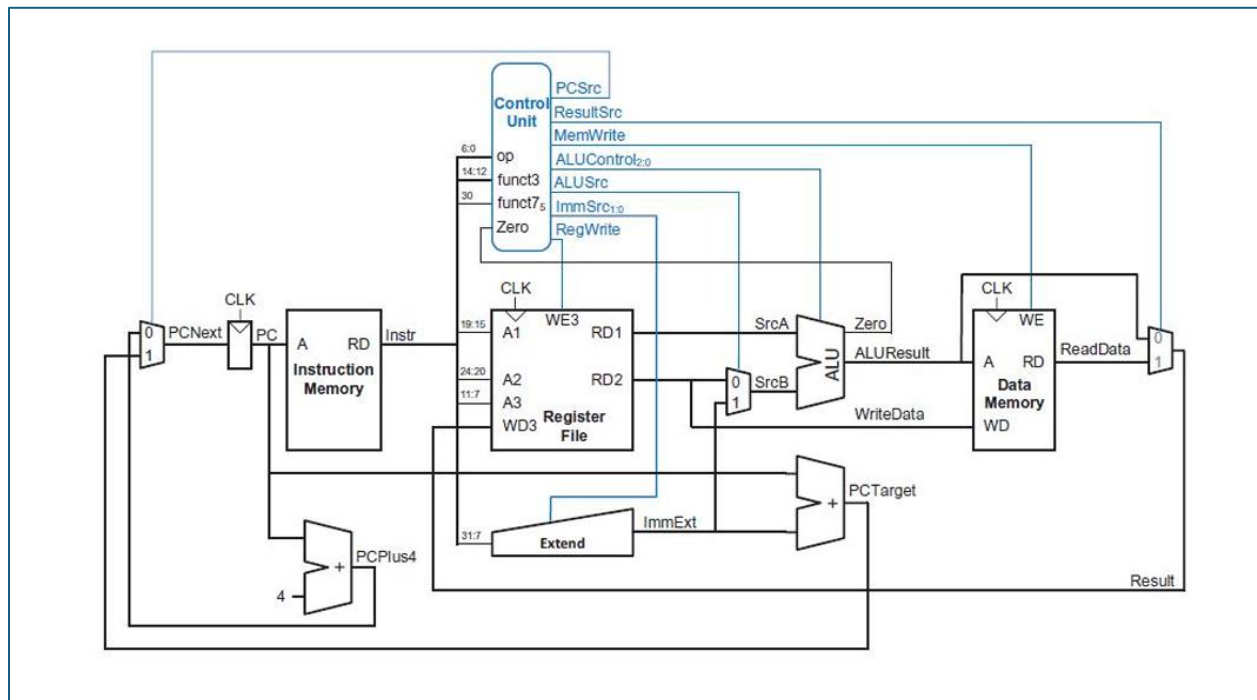


Figure 1 Complete single-cycle RISC-V processor

ALU Module:

```
module ALU (  
    input wire [31:0] SrcA,           // First 32-bit input operand  
    input wire [31:0] SrcB,           // Second 32-bit input operand  
    input wire [2:0] ALUControl,      // Control signal to select ALU operation  
    output wire Zero,                 // Output flag: HIGH if ALUResult == 0  
    output wire signflag,  
    // Output flag: Sign bit of the result (MSB of ALUResult)  
    output reg [31:0] ALUResult  
    // Final 32-bit result of the ALU operation  
);  
  
    // Combinational logic block  
    always @(*)  
    begin  
        case (ALUControl)  
            3'b000: ALUResult = SrcA + SrcB; // Addition  
            3'b001: ALUResult = SrcA << SrcB; // Logical left shift  
            3'b010: ALUResult = SrcA - SrcB; // Subtraction  
            3'b100: ALUResult = SrcA ^ SrcB; // Bitwise XOR  
            3'b101: ALUResult = SrcA >> SrcB; // Logical right shift  
            3'b110: ALUResult = SrcA | SrcB; // Bitwise OR  
            3'b111: ALUResult = SrcA & SrcB; // Bitwise AND  
            default: ALUResult = 32'd0; // Default: Output zero  
        endcase  
    end  
  
    // Zero flag: Set HIGH if the ALU result is 0  
    assign Zero = (ALUResult == 32'd0);  
  
    // Sign flag: MSB of the ALU result (1 if negative in signed representation)  
    assign signflag = ALUResult[31];  
endmodule
```

PC Counter Module:

```
module PC_COUNTER (
    input wire CLK,           // Clock signal
    input wire RST,           // Active-low reset signal
    input wire [31:0] PCNext, // Next PC value (input from instruction logic)
    output reg [31:0] PC      // Current PC value (program counter output)
);

// Sequential block triggered on rising edge of clock or falling edge of reset
always @(posedge CLK or negedge RST)
begin
    if (!RST)
        begin
            // If reset is asserted (active-low), reset PC to 0
            PC <= 32'd0;
        end
    else
        begin
            // Otherwise, load next PC value
            PC <= PCNext;
        end
    end
end

endmodule
```

Instruction memory:

```
module INSTRUCTION_MEMORY (
    input wire [31:0] A, // PC
    output wire [31:0] RD // instruction
);
    // 64 words * 32 bits = 2 KB
    reg [31:0] ROM [0:63];

    // asynchronous read (word-aligned)
    assign RD = ROM[A[31:2]];

    // optional: preload program
endmodule
```

Register File:

```
module Register_file (
    input wire      CLK,      // Clock
    input wire      RST,      // Reset (active-low)
    input wire      WE3,      // Write enable
    input wire [31:0] WD3,    // Write data
    input wire [4:0] A1,      // Read address 1
    input wire [4:0] A2,      // Read address 2
    input wire [4:0] A3,      // Write address
    output wire [31:0] RD1,    // Read data 1
    output wire [31:0] RD2    // Read data 2
);

    // Register file: 32 registers, each 32-bit wide
    reg [31:0] File [0:31];
    integer i;

    // Sequential logic for reset and write operations
    always @(posedge CLK or negedge RST)
    begin
        if (!RST) begin
            // Asynchronous reset: clear all registers to 0
            for (i = 0; i < 32; i = i + 1)
                File[i] <= 32'd0;
        end
        else if (WE3 && A3 != 5'd0) begin
            // Write data WD3 into register A3
            // (writing to register 0 is not allowed)
            File[A3] <= WD3;
        end
    end

    // Combinational read ports
    assign RD1 = File[A1];    // Read data from register at address A1
    assign RD2 = File[A2];    // Read data from register at address A2

endmodule
```

Data Memory:

```
module DATA_memory (
    input wire      CLK,      // Clock
    input wire      RST,      // Reset (active-low)
    input wire      WE,       // Write enable
    input wire [31:0] A,       // Address (word-aligned)
    input wire [31:0] WD,      // Write data
    output wire [31:0] RD      // Read data
);

    // 64 words of memory, each word is 32-bit wide
    reg [31:0] Dmemory [0:63];
    integer i;

    // Sequential logic for reset and write
    always @(posedge CLK or negedge RST)
    begin
        if (!RST) begin
            // Reset: clear entire memory to 0
            for (i = 0; i < 64; i = i + 1)
                Dmemory[i] <= 32'd0;
        end
        else if (WE) begin
            // Write operation (word-aligned: ignore lowest 2 address bits)
            Dmemory[A[31:2]] <= WD;
        end
    end

    // Combinational read (word-aligned)
    assign RD = Dmemory[A[31:2]];

endmodule
```

ControlUnit:

```
module ControlUnit (
    input wire Zero,      // Zero flag from ALU
    input wire sign,      // Sign flag from ALU
    input wire [6:0] OP,   // Opcode field from instruction
    input wire [2:0] funct3, // funct3 field
    input wire funct7,     // funct7 bit (for R-type instructions)

    output reg [2:0] ALUControl, // ALU operation select
    output reg PCSrc,           // Program counter source (branch control)
    output reg ResultSrc,       // Selects ALU result or memory read
    output reg MemWrite,        // Memory write enable
    output reg ALUSrc,          // Selects between register or immediate for ALU input
    output reg [1:0] ImmSrc,     // Immediate type (I, S, B, etc.)
    output reg RegWrite         // Register file write enable
);

// Internal signals
reg [1:0] ALUOP; // ALU operation type control
reg Branch; // Branch flag

wire bnq; // Branch if not equal
wire blt; // Branch if less than
wire beq; // Branch if equal

//=====
// Main Decoder: Sets control signals based on opcode
//=====
always @(*)
begin
    casex (OP)
        // Load (I-type)
        7'b000_0011: begin
            RegWrite = 1'b1;
            ImmSrc = 2'b00;
            ALUSrc = 1'b1;
            MemWrite = 1'b0;
            ResultSrc = 1'b1;
            Branch = 1'b0;
            ALUOP = 2'b00;
        end

        // Store (S-type)
        7'b010_0011: begin
            RegWrite = 1'b0;
            ImmSrc = 2'b01;
            ALUSrc = 1'b1;
            MemWrite = 1'b1;
            ResultSrc = 1'bx;
            Branch = 1'b0;
            ALUOP = 2'b00;
        end
    end
end
```

```

// R-type
7'b011_0011: begin
    RegWrite = 1'b1;
    ImmSrc   = 2'bxx;
    ALUSrc   = 1'b0;
    MemWrite = 1'b0;
    ResultSrc = 1'b0;
    Branch   = 1'b0;
    ALUOP    = 2'b10;
end

// I-type (ALU immediate)
7'b001_0011: begin
    RegWrite = 1'b1;
    ImmSrc   = 2'b00;
    ALUSrc   = 1'b1;
    MemWrite = 1'b0;
    ResultSrc = 1'b0;
    Branch   = 1'b0;
    ALUOP    = 2'b10;
end

// B-type (branch)
7'b110_0011: begin
    RegWrite = 1'b0;
    ImmSrc   = 2'b10;
    ALUSrc   = 1'b0;
    MemWrite = 1'b0;
    ResultSrc = 1'bx;
    Branch   = 1'b1;
    ALUOP    = 2'b01;
end

// Default: do nothing
default: begin
    RegWrite = 1'b0;
    ImmSrc   = 2'b00;
    ALUSrc   = 1'b0;
    MemWrite = 1'b0;
    ResultSrc = 1'b0;
    Branch   = 1'b0;
    ALUOP    = 2'b00;
end
endcase
end

//=====
// ALU Decoder: Selects exact ALU operation
//=====
always @(*)
begin
    casex ({ALUOP, funct3, OP[5], funct7})
        7'b00_xxx_x_x: ALUControl = 3'b000; // Default: ADD
        7'b01_000_x_x: ALUControl = 3'b010; // BEQ: Subtract
        7'b01_001_x_x: ALUControl = 3'b010; // BNE: Subtract
        7'b01_100_x_x: ALUControl = 3'b010; // BLT: Subtract
        7'b10_000_0_0: ALUControl = 3'b000; // ADD
        7'b10_000_0_1: ALUControl = 3'b000; // ADD
        7'b10_000_1_0: ALUControl = 3'b000; // ADD
        7'b10_000_1_1: ALUControl = 3'b010; // SUB
        7'b10_001_x_x: ALUControl = 3'b001; // SLL
        7'b10_100_x_x: ALUControl = 3'b100; // XOR
        7'b10_101_x_x: ALUControl = 3'b101; // SRL
        7'b10_110_x_x: ALUControl = 3'b110; // OR
        7'b10_111_x_x: ALUControl = 3'b111; // AND
        default:      ALUControl = 3'b000;
    endcase
end

//=====
// Branch decision logic
//=====
assign beq = Branch & Zero; // Branch if equal
assign bnq = Branch & ~Zero; // Branch if not equal
assign blt = Branch & sign; // Branch if less than

always @(*)
begin
    if (ALUOP == 2'b01) begin
        case (funct3)
            3'b000: PCSrc = beq; // BEQ
            3'b001: PCSrc = bnq; // BNE
            3'b100: PCSrc = blt; // BLT
            default: PCSrc = 1'b0;
        endcase
    end
    else
        PCSrc = 1'b0; // No branch
    end
end
endmodule

```


Signed Extend:

```
1 module sign_extend (
2     input wire [31:0] Instr ,    // Full 32-bit instruction
3     input wire [1:0] ImmSrc ,    // Control signal to select immediate type
4     output reg [31:0] ImmExt     // Sign-extended immediate output
5 );
6
7 always @(*)
8 begin
9     case (ImmSrc)
10        // I-type immediate (12 bits from [31:20])
11        // Example: addi, lw
12        2'b00:
13            ImmExt = {{20{Instr[31]}}, Instr[31:20]};
14
15        // S-type immediate (12 bits from [31:25] & [11:7])
16        // Example: sw
17        2'b01:
18            ImmExt = {{20{Instr[31]}}, Instr[31:25], Instr[11:7]};
19
20        // B-type immediate (branch offset, 13 bits)
21        // Immediate fields: Instr[31], Instr[7], Instr[30:25], Instr[11:8], plus 0 at LSB
22        // Example: beq, bne
23        2'b10:
24            ImmExt = {{20{Instr[31]}}, Instr[7], Instr[30:25], Instr[11:8], 1'b0};
25
26        // Default case -> no immediate
27        default:
28            ImmExt = 32'd0;
29    endcase
30 end
31 endmodule
32
```

Mux:

```
1 module mux2_1 (  
2     input wire [31:0] In1,  
3     input wire [31:0] In2,  
4     input wire sel,  
5     output reg [31:0] out  
6 );  
7     always @(*)  
8     begin  
9         if(!sel)  
10            out = In1;  
11        else  
12            out = In2;  
13        end  
14 endmodule
```

Adder:

```
module Adder (  
    input wire [31:0] A,  
    input wire [31:0] B,  
    output wire [31:0] out  
);  
    assign out = A + B;  
endmodule
```

Risc Top Module:

```
1 module RISC (
2     input wire CLK,      // Clock
3     input wire RST       // Reset (active-low)
4 );
5
6 // Control signals
7 wire RegWrite;           // Register write enable
8 wire [1:0] ImmSrc;       // Immediate source type
9 wire ALUSrc;             // Select between register or immediate for ALU operand B
10 wire [2:0] ALUControl;   // ALU operation control
11 wire MemWrite;          // Memory write enable
12 wire ResultSrc;         // Select between ALU result or memory read for write-back
13 wire PCSrc;             // Select between PC+4 or branch target
14
15 // Status flags
16 wire Zero;              // Zero flag from ALU
17 wire sign;              // Sign flag from ALU
18
19 // Data path wires
20 wire [31:0] Result;      // Final result written back to register file
21 wire [31:0] Instr;       // Current instruction
22 wire [31:0] SrcA;        // ALU operand A (from register file)
23 wire [31:0] SrcB;        // ALU operand B (from register file or immediate)
24 wire [31:0] PC;         // Current program counter
25 wire [31:0] PCNext;     // Next program counter value
26 wire [31:0] PCTarget;   // Branch target address
27 wire [31:0] ALUResult;  // Result from ALU
28 wire [31:0] WriteData;  // Data to be written into memory
29 wire [31:0] ReadData;   // Data read from memory
30 wire [31:0] ImmExt;     // Sign-extended immediate value
31 wire [31:0] PCPlus4;    // PC + 4 (next sequential instruction)
32
33 // ----- Control Unit -----
34 ControlUnit DUT
35 (
36     .Zero(Zero),
37     .sign(sign),
38     .OP(Instr[6:0]),
39     .funct3(Instr[14:12]),
40     .funct7(Instr[30]),
41     .ALUControl(ALUControl),
42     .PCSrc(PCSrc),
43     .ResultSrc(ResultSrc),
44     .MemWrite(MemWrite),
45     .ALUSrc(ALUSrc),
46     .ImmSrc(ImmSrc),
47     .RegWrite(RegWrite)
48 );
49
```

```

// ----- Instruction Memory -----
INSTRUCTION_MEMORY DUT2
(
    .A(PC),
    .RD(Instr)
);

// ----- Program Counter -----
PC_COUNTER DUT3
(
    .CLK(CLK),
    .RST(RST),
    .PCNext(PCNext),
    .PC(PC)
);

// ----- PC + 4 Adder -----
Adder DUT11
(
    .A(PC),
    .B(32'd4),
    .out(PCPlus4)
);

// ----- PC Mux (Next PC: sequential or branch) -----
mux2_1 DUT12
(
    .In1(PCPlus4),
    .In2(PCTarget),
    .sel(PCSrc),
    .out(PCNext)
);

// ----- ALU -----
ALU DUT5
(
    .SrcA(SrcA),
    .SrcB(SrcB),
    .ALUControl(ALUControl),
    .Zero(Zero),
    .signflag(sign),
    .ALUResult(ALUResult)
);

// ----- Data Memory -----
DATA_memory DUT6
(
    .CLK(CLK),
    .RST(RST),
    .WE(MemWrite),
    .A(ALUResult),
    .WD(WriteData),
    .RD(ReadData)
);

// ----- Immediate Generator -----
sign_extend DUT7
(
    .Instr(Instr),
    .ImmSrc(ImmSrc),
    .ImmExt(ImmExt)
);

// ----- Branch Target Adder -----
Adder DUT8
(
    .A(PC),
    .B(ImmExt),
    .out(PCTarget)
);

// ----- Result Mux (Write-back: ALU or Memory) -----
mux2_1 DUT9
(
    .In1(ALUResult),
    .In2(ReadData),
    .sel(ResultSrc),
    .out(Result)
);

// ----- ALU Src Mux (Operand B: Register or Immediate) -----
mux2_1 DUT10
(
    .In1(WriteData),
    .In2(ImmExt),
    .sel(ALUSrc),
    .out(SrcB)
);

endmodule

```

Simple TB :

To check FIBONACCI series

```
module RISC_tb;
    reg CLK, RST;

    RISC dut (
        .CLK(CLK),
        .RST(RST)
    );

    always #5 CLK = ~CLK; // 100 MHz clock

    initial begin
        // Initialize clock/reset
        CLK = 0;
        RST = 0;

        // Load program into instruction memory
        $readmemh("program.mem", dut.DUT2.ROM);

        #20 RST = 1; // release reset

        // Run long enough
        #2000 $stop;
    end
endmodule
```

Results:

 


Figure2 Waveform

Elaborated Design:

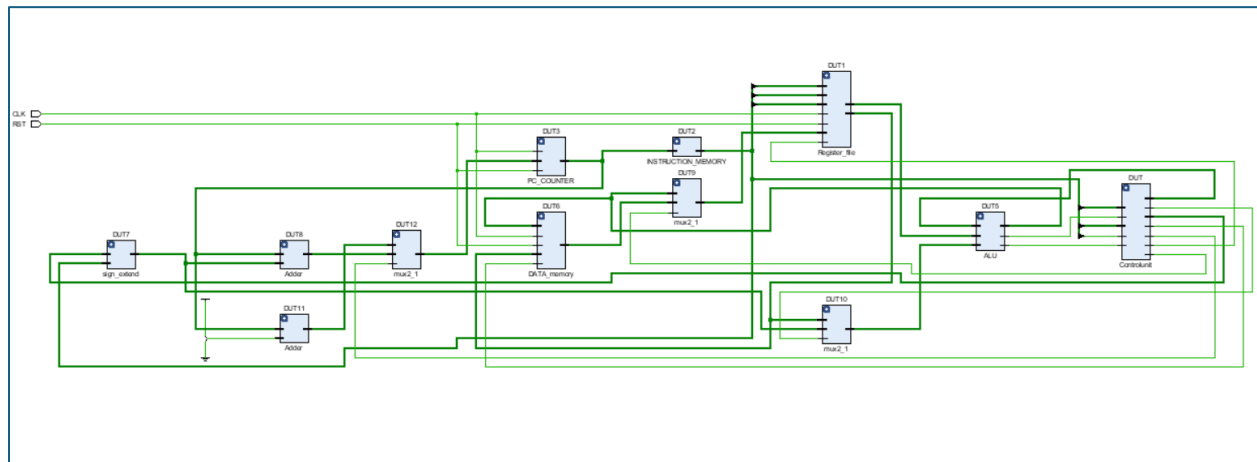


Figure 3 Elaborated Design